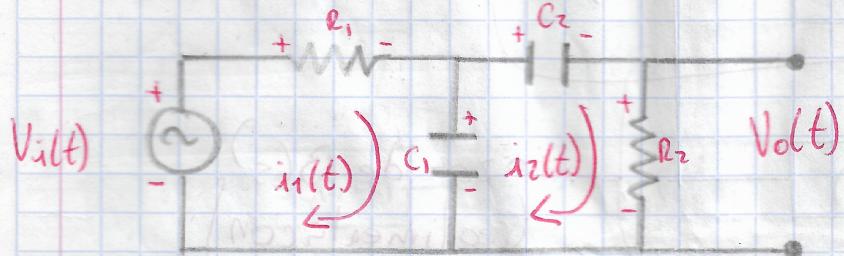


Tarea Instrumentación

F.T. del filtro pasa banda con D.B.



$$V_{in}(t) = R_1 i_1(t) + \frac{1}{C_1} \int i_1(t) dt - \frac{1}{C_1} \int i_2(t) dt$$

$$\phi = \frac{1}{C_1} \int i_2(t) dt - \frac{1}{C_1} \int i_1(t) dt + \frac{1}{C_2} \int i_2(t) dt + R_2 i_2(t)$$

$$V_{out}(t) = R_2 i_2(t)$$

$$V_{in}(s) = R_1 I_1(s) + \frac{1}{sC_1} I_1(s) - \frac{1}{sC_1} I_2(s)$$

$$\phi = \frac{1}{sC_1} I_2(s) - \frac{1}{sC_1} I_1(s) + \frac{1}{sC_2} I_2(s) + R_2 I_2(s)$$

V.S $(V_{out}(s)) = R_2 I_2(s)$ V.F

$$\phi = I_2(s) \left(\frac{1}{sC_1} + \frac{1}{sC_2} + R_2 \right) - \frac{1}{sC_1} I_1(s)$$





V.S $(I_1(s)) = I_2(s) \left(\frac{(C_2 + C_1 + sC_1 sC_2 R_2)}{sC_2} \right)$ F.T

$$V_{in}(s) = I_1(s) \left(R_1 + \frac{1}{sC_1} \right) - \frac{1}{sC_1} I_2(s)$$


$$I_2(s) = I_1(s) \left(R_1 + \frac{1}{sC_1} \right) - V_{in}(s)$$

$$I_2(s) = (I_1(s) \left(R_1 + \frac{1}{sC_1} \right) - V_{in}(s)) sC_1$$

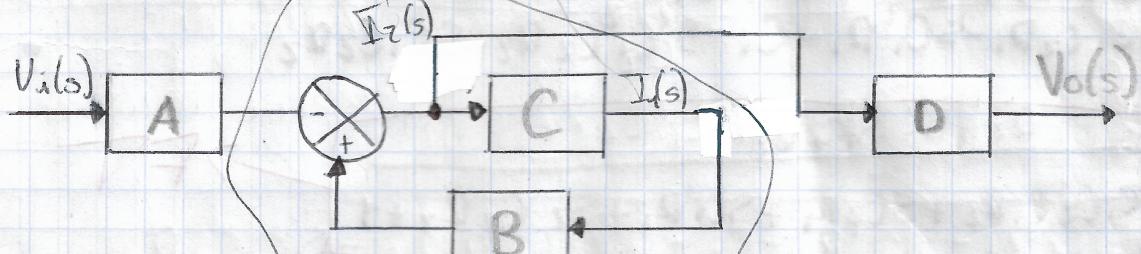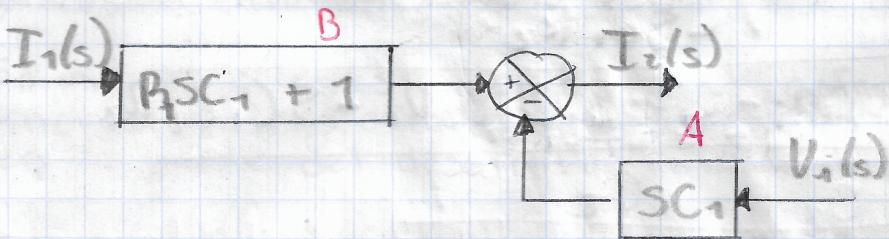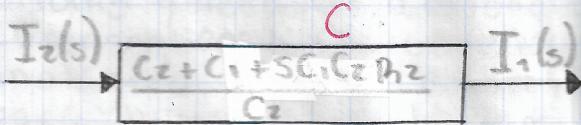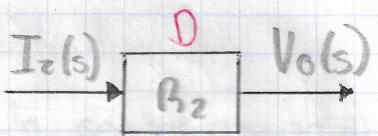V.S $(I_2(s)) = I_1(s) \left((R_1 sC_1 + 1) - \frac{V_{in}(s)}{sC_1} \right)$ F.T V.F




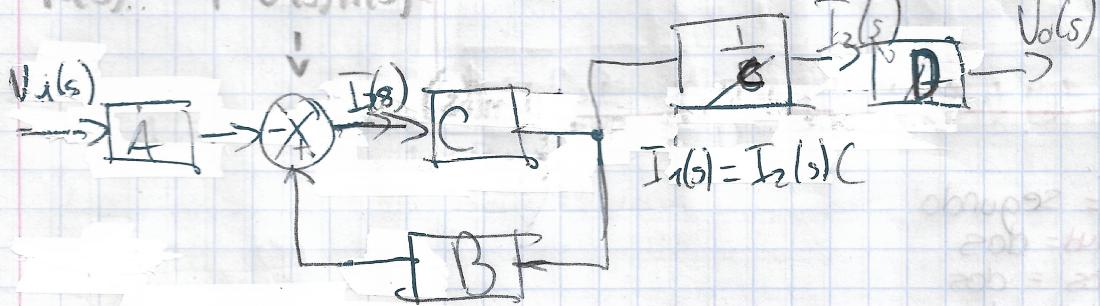
$$\frac{C(s)}{R(s)} = \frac{-G(s)}{1 - G(s)H(s)}$$



$$I_1(s) = I_2(s)C$$

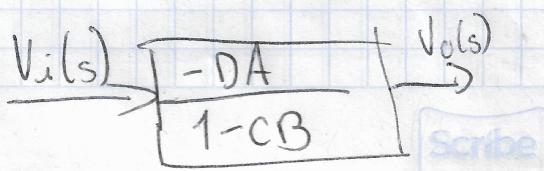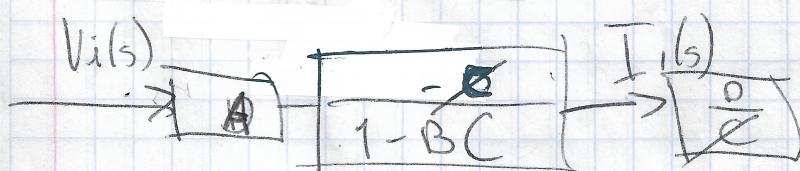obrigos
eob - utinox
eob = 210 311
eob = 2050 311



$$\frac{-AD}{1-BC}$$

$$\begin{aligned}
 &= \frac{-Sc_1R_2}{C_2 + C_1 + SC_1C_2R_2} \\
 &= \frac{1 - \frac{C_2 + C_1 + SC_1C_2R_2}{C_2}}{1 - \frac{C_1}{C_2}} \cdot \frac{-Sc_1R_2}{C_2} \\
 &= \frac{-SC_1C_2R_2 - SC_1^2R_1 - C_1 - S^2C_1^2C_2R_2 - SC_1C_2R_2}{C_2} \\
 &= -\frac{SC_1C_2R_2}{SC_1C_2R_2 - SC_1^2R_1 - C_1 - S^2C_1^2C_2R_2 - SC_1C_2R_2} \\
 &= \boxed{\frac{SC_1R_2}{S^2C_1C_2R_1R_2 + SC_2R_1 + SC_1R_1 + SC_2C_2R_2 + 1}} \rightarrow FT
 \end{aligned}$$

Orden = Segundo
 Exactitud = dos
 No. polos = dos
 No. ceros = dos