

## Práctica 13: Decodificadores

Nombre: Colín Ramiro Joel


No. de lista: 3

### **Ejercicio 1.-**

*Implemente teóricamente un decodificador 4x16 mediante el uso de decodificadores de 3x8*

[illegible]

<b>E2</b>	<b>E1</b>	<b>E0</b>	<b>A</b>	<b>S7</b>	<b>S6</b>	<b>S5</b>	<b>S4</b>	<b>S3</b>	<b>S2</b>	<b>S1</b>	<b>S0</b>
0	0	0	1	0	0	0	0	0	0	0	1
0	0	1	1	0	0	0	0	0	0	1	0
0	1	0	1	0	0	0	0	0	1	0	0
0	1	1	1	0	0	0	0	1	0	0	0
1	0	0	1	0	0	0	1	0	0	0	0
1	0	1	1	0	0	1	0	0	0	0	0
1	1	0	1	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0
X	X	X	0	0	0	0	0	0	0	0	0

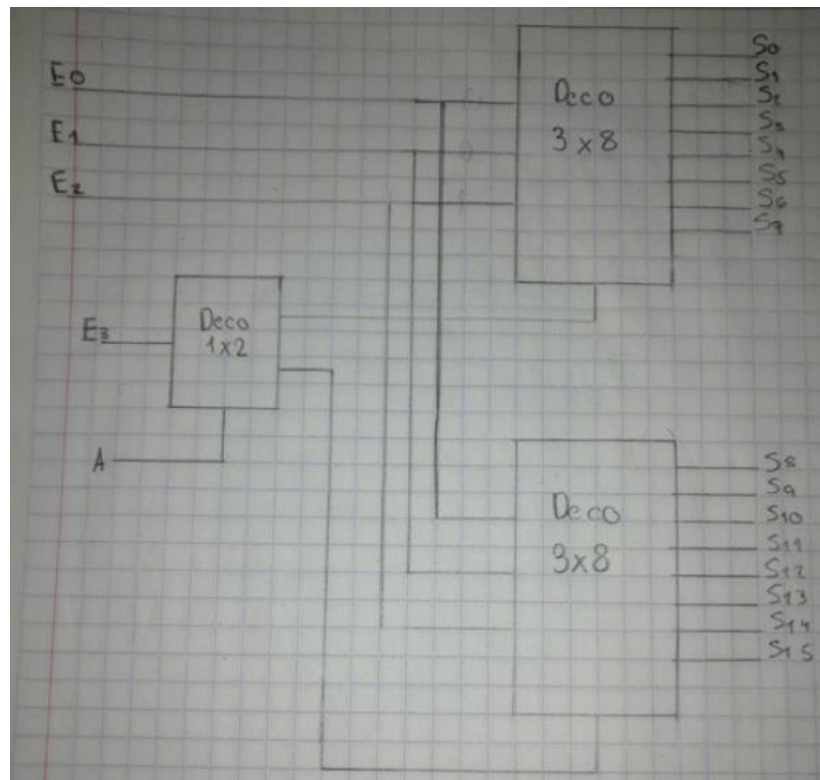

### **Ejercicio 2.-**

Realizar la simulación para obtener los resultados de la siguiente tabla:

SAL(3)	SAL(2)	SAL(1)	SAL(0)	SAL2(3)	SAL2(2)	SAL2(1)	SAL2(0)
0	0	1	0	0	1	0	0
1	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	0	0	1	0	0	0

## Código ejercicio 2.-

```

library ieee;
use ieee.std_logic_1164.all;
entity parte1 is
port(
    ent: in std_logic_vector(1 downto 0);
    Z,Y: in std_logic;
    sal,sal2:out std_logic_vector(3 downto 0)
);
end parte1;
architecture aparte1 of parte1 is
begin

    process(ent,Z)
    begin
        if(Z = '1')then
            if (ent = "00")then
                sal <= "0001";
            elsif (ent = "01")then
                sal <= "0010";
            elsif (ent = "10")then
                sal <= "0100";
            else
                sal <= "1000";
            end if;
        else
            sal <= "0000";
        end if;
    end process;

    -----
    process(ent,Y)
    begin
        if (Y = '1')then
            case ent is
                when "00" => sal2 <= "0001";
                when "01" => sal2 <= "0100";
                when "10" => sal2 <= "0010";
                when "11" => sal2 <= "1000";
                when others => sal2 <= "1XXX";
            end case;
        end if;
    end process;
end aparte1;

```

```

        end case;
    else
        sal2 <= "0000";
    end if;
end process;
end aparte1;

```



## Ecuaciones ejercicio 2.-




```

sal(0) =
    /ent(0) * /ent(1) * z
sal(1) =
    ent(0) * /ent(1) * z
sal(2) =
    /ent(0) * ent(1) * z
sal(3) =
    ent(0) * ent(1) * z
sal2(0) =
    /ent(0) * /ent(1) * y
sal2(1) =
    /ent(0) * ent(1) * y
sal2(2) =
    ent(0) * /ent(1) * y
sal2(3) =
    ent(0) * ent(1) * y


```





## Simulación VHDL ejercicio 2.-

 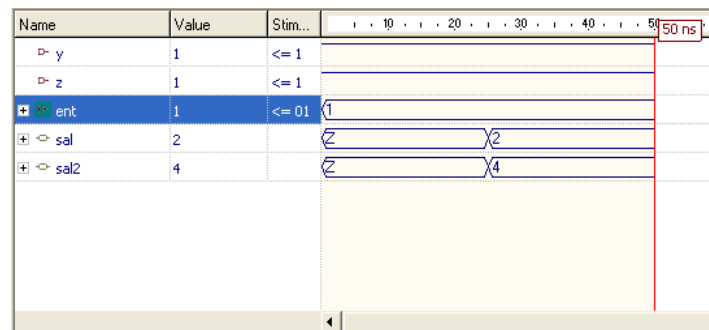

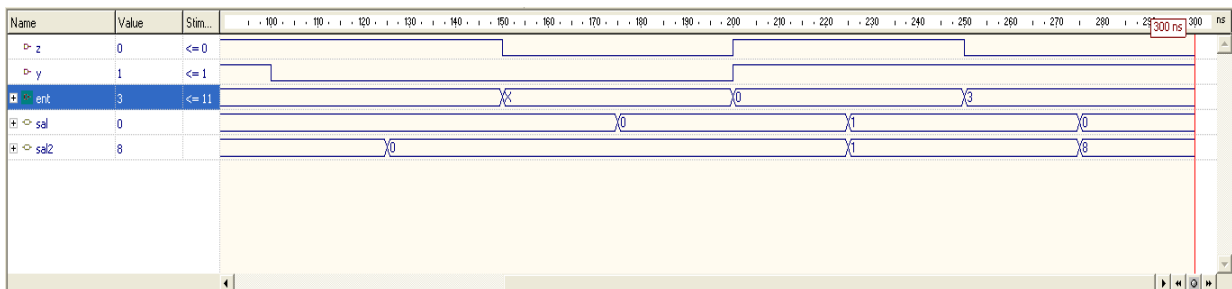 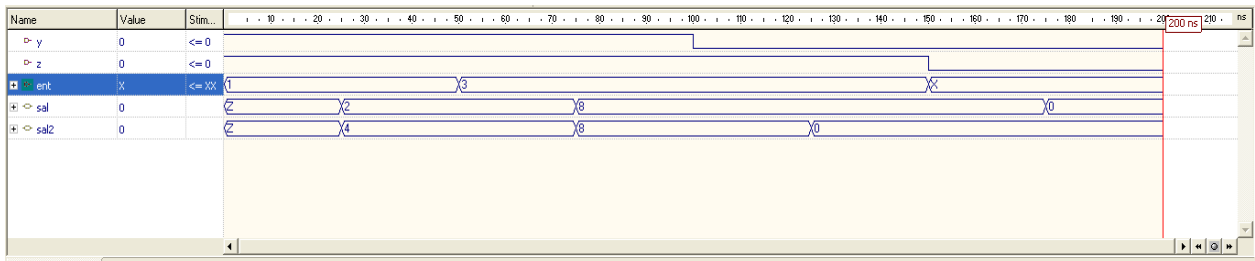

## Simulación en Proteus ejercicio 2.-

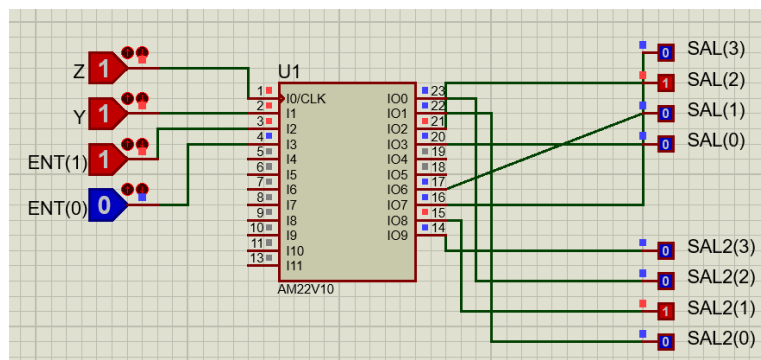

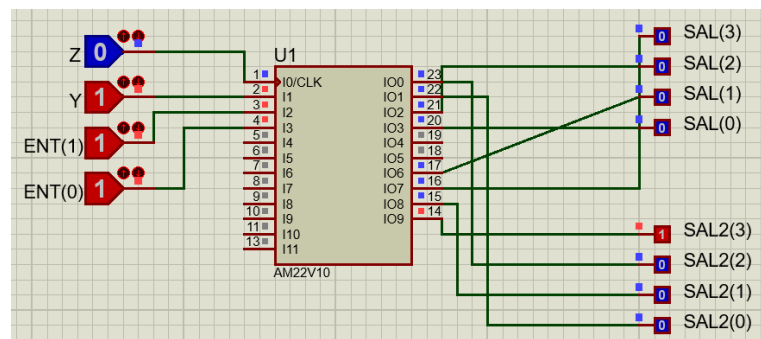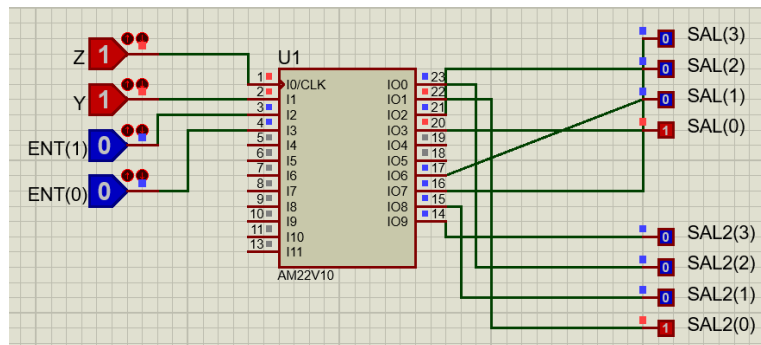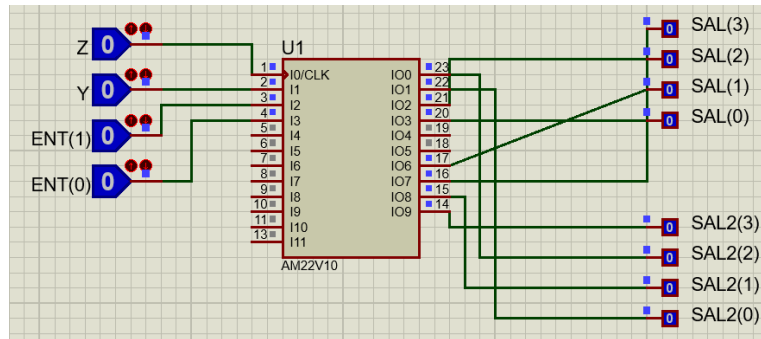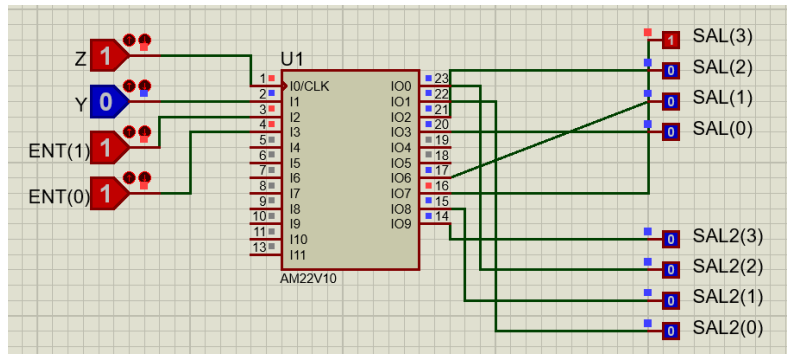

**Ejercicio 3:** Implementar en VHDL un decodificador 3x8 mediante decodificadores 2x4 con señal de habilitación, usando los niveles de descripción que no se usaron en el ejercicio 2.

### ***Código ejercicio 3.-***

```
library ieee;
use ieee.std_logic_1164.all;
entity parte2 is
port(
    ent: in std_logic_vector(1 downto 0);
    A,E2:in std_logic;
    sal,sal2:out std_logic_vector(3 downto 0)

);
end parte2;
architecture aparte2 of parte2 is
signal C,D:std_logic;
signal sal3:std_logic_vector(3 downto 0);
begin

    C <= '1' when(E2 = '0')else
        '0';
        sal <=
            "0001" when(ent = "00" AND C ='1')else
            "0010" when(ent = "01" AND C ='1')else
            "0100" when(ent = "10" AND C ='1')else
            "1000" when(ent = "11" AND C ='1')else
            "0000" when (C='0') else
            "ZZZZ";

-----

    D <= '1' when(E2 = '1')else
        '0';
        with ent select sal3 <=
            "0001" when "00",
            "0010" when "01",
            "0100" when "10",
            "1000" when "11",
            "0000" when others;

        with D select sal2 <=
            sal3 when '1',
            "0000" when '0',
            "XXXX" when others;

end aparte2;
```



### Ecuaciones ejercicio 3.-

```






sal(0) =
    /e2 * /ent(0) * /ent(1)
sal(1) =
    /e2 * ent(0) * /ent(1)
sal(2) =
    /e2 * /ent(0) * ent(1)
sal(3) =
    /e2 * ent(0) * ent(1)
sal2(0) =
    e2 * /ent(0) * /ent(1)
sal2(1) =
    e2 * ent(0) * /ent(1)
sal2(2) =
    e2 * /ent(0) * ent(1)
sal2(3) =
    e2 * ent(0) * ent(1)



```

### Simulación en VHDL ejercicio 3.-

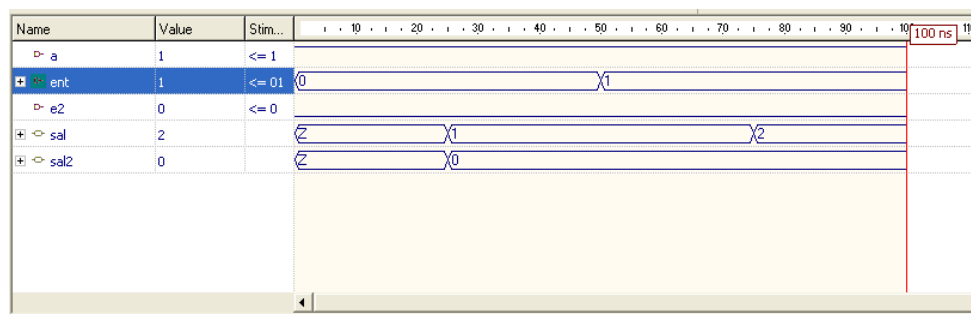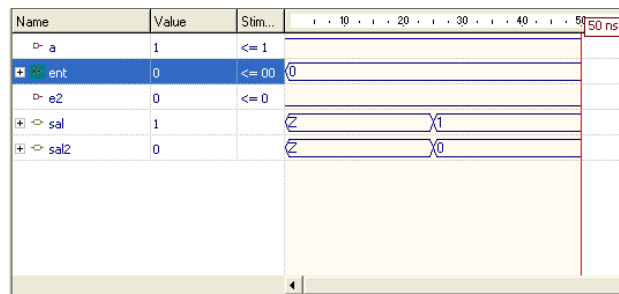



    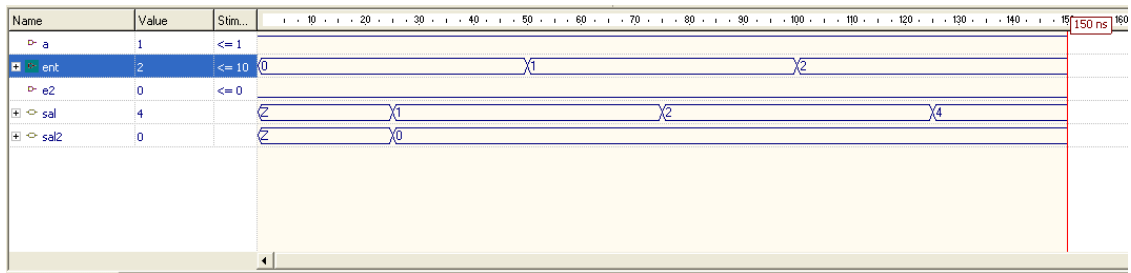

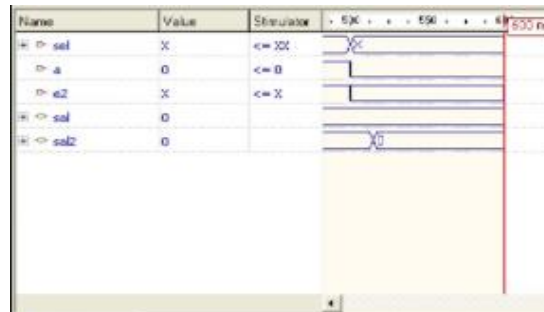 

### Simulación en Proteus ejercicio 3.-

